



Ch—07 Alternating Current

Daily Practice Problem 04

Q1. When an inductor L and a resistor R in series are connected across a 12 V , 50 Hz supply, a current of 0.5 A flows in the circuit. The current differs in phase from applied voltage by $\pi/3$ radian. Calculate the value of R .


Q2. A bulb of resistance $10\ \Omega$, connected to an inductor of inductance L , is in series with an a.c. source marked 100 V , 50 Hz . If the phase angle between the voltage and current is 4 radian , calculate the value of L .

Q3. A student connects a long air core coil of manganin wire to a 100 V d.c. source and records a current of 1.5 A . When the same coil is connected across 100 V , 50 Hz a.c. source the current reduces to 1.0 A .

- (i) Give reason for this observation.
- (ii) Calculate the value of the reactance of the coil.

Q4. In the circuit shown in Fig., the potential difference across the inductor L and resistor R are 120 V and 90 V respectively and the *rms* value of current is 3 A . Calculate

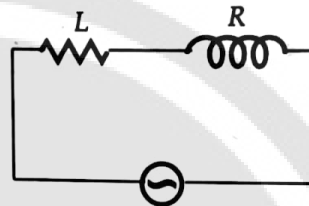- (i) the impedance of the circuit and
- (ii) the phase angle between the voltage and current.




Q5. When 100 V dc is supplied across a solenoid, a current of 1.0 A flows in it. When 100 V ac is applied across the same coil, the current drops 0.5 A . the frequency of ac source is 50 Hz , then the impedance and inductance of the solenoid are

- (a) $200\ \Omega$ and 0.55 H
- (b) $100\ \Omega$ and 0.86 H
- (c) $200\ \Omega$ and 1.0 H
- (d) $100\ \Omega$ and 0.93 H

Q6. The virtual current in the a.c. circuit shown in Fig., is 1.0 A . Find

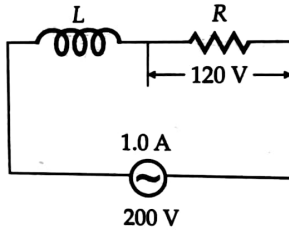- (i) virtual voltage across the coil L ,
- (ii) impedance of the circuit and
- (iii) reactance of the coil.



Q7. Find the impedance of the circuit shown in Fig., for

- (i) direct current and
- (ii) alternating current of frequency $10/\pi$ kHz.



Q8. In a series R-C circuit, $R = 30 \Omega$, $C = 0.25 \mu F$, $V = 100 V$ and $\omega =$

$10,000 \text{ rad s}^{-1}$. Find the current in the circuit and calculate the voltage across the resistor and the capacitor.

Q9. A series circuit contains a resistor of 20Ω , a capacitor and an ammeter of negligible resistance. It is connected to a source of $220 V - 50 \text{ Hz}$. If the reading of the ammeter is $2.5 A$, calculate the reactance of the capacitor.

Q10. What is the value of current in the a.c. circuit containing $R = 10 \Omega$, $C = 50 \mu F$ in series across $200 V$, 50 Hz a.c. source?

ANSWERS

1. $12\ \Omega$
2. $0.0318\ H$
3. $74.53\ \Omega$
4. $50\ \Omega$; 53.1°
5. a
6. (i) $160\ V$
(ii) $200\ \Omega$
(iii) $160\ \Omega$
7. (i) infinite (ii) $32\ \Omega$
8. $0.25\ A$; $7.5\ V$; $100\ V$
9. $85.7\ \Omega$
10. $3.10\ A$