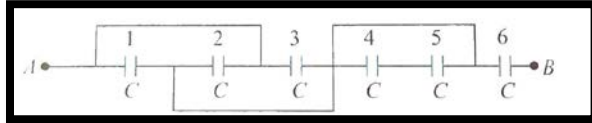



## Ch—02 Electrostatic Potential and Capacitance

### Daily Practice Problem 08


**Q1.** Find the equivalent capacitance between points A and B as shown in figure.



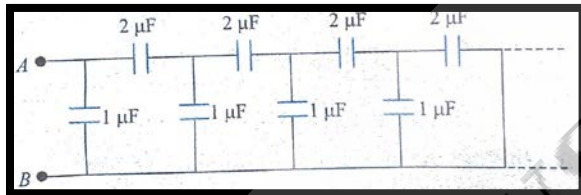
**Q2.** Find the equivalent capacitance of the infinite ladder shown in figure between the points A and B.



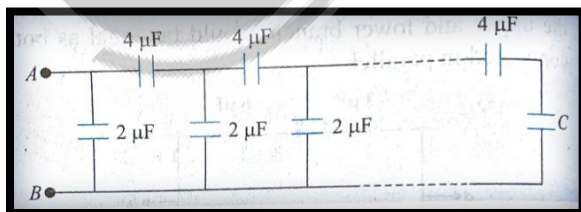**Q3.** An infinite ladder is constructed by connecting several sections, of  $2\ \mu\text{F}$ ,  $4\ \mu\text{F}$  capacitor combinations as shown in figure. It is terminated by a capacitor of capacitance  $C$ . What value should be chosen for  $C$  such that the equivalent capacitance of the ladder between A and B becomes independent of the number of sections in between?




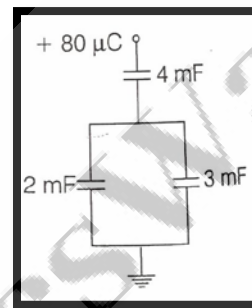**Q4.** In the given circuit, a charge of  $+80\ \mu\text{C}$  is given to the upper plate of the  $4\ \mu\text{F}$  capacitor. Then in the steady state, the charge on the upper plate of the  $3\ \mu\text{F}$  capacitor is




- a.  $+32\ \mu\text{C}$
- b.  $+40\ \mu\text{C}$
- c.  $+48\ \mu\text{C}$
- d.  $+80\ \mu\text{C}$

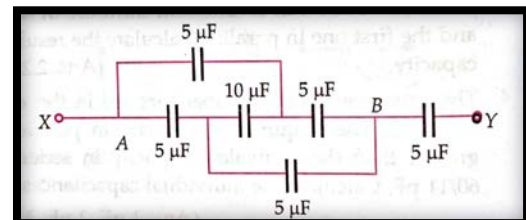
**Q5.** Find the resultant capacitance between the points X and Y of the combination of capacitors shown in Fig.



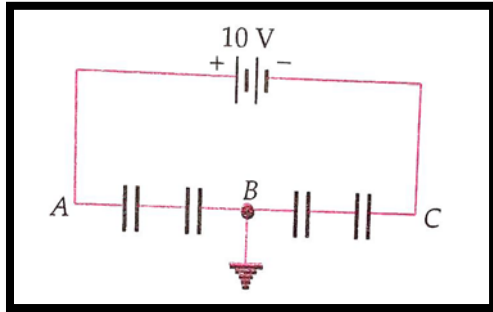
**Q6.** Four capacitors of equal capacitances are connected in series with a battery of 10 V, as shown in Fig. The middle point B is connected to the earth. What will be the potentials of the points A and C?



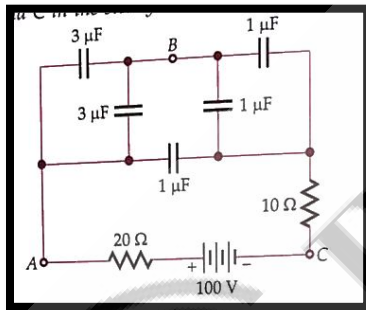
**Q7.** For the network shown in Fig., find the potential difference between points A and B, and that between B and C in the steady state.



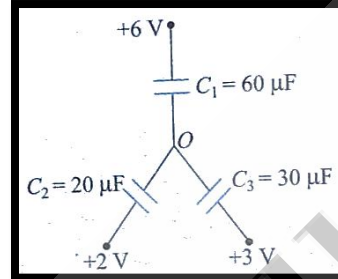**Q8.** Three uncharged capacitors of capacitance  $C_1$ ,  $C_2$  and  $C_3$  are connected to one another as shown in figure. Find the potential at O.



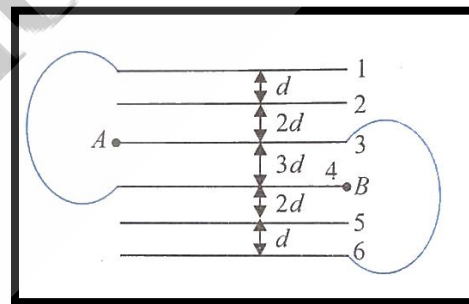**Q9.** Six plates of equal area  $A$  and plate separation as shown (figure) are arranged. The equivalent capacitance between A and B is




a.  $\frac{\epsilon_0 A}{d}$

b.  $\frac{2\epsilon_0 A}{d}$

c.  $\frac{3\epsilon_0 A}{d}$


d.  $\frac{\epsilon_0 A}{4d}$

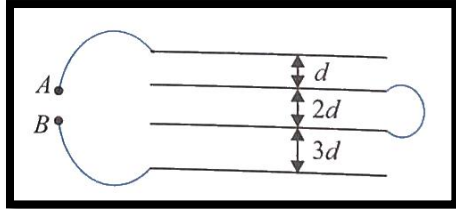**Q10.** If area of each plate is  $A$  and the successive separations are  $d$ ,  $2d$ , and  $3d$ , then the equivalent capacitance across  $A$  and  $B$  is



- a.  $\frac{\epsilon_0 A}{6d}$       b.  $\frac{\epsilon_0 A}{4d}$   
 c.  $\frac{3\epsilon_0 A}{4d}$       d.  $\frac{\epsilon_0 A}{3d}$

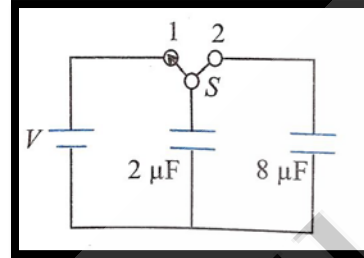**Q11.** A  $2\ \mu\text{F}$  capacitor is charged as shown in the figure. The percentage of its stored energy dissipated after switch  $S$  is turned to position 2 is



- a. 0%  
 b. 20%  
 c. 75%  
 d. 80%

## ANSWERS

1.  $3C/4$
2.  $2\ \mu\text{F}$
3.  $C = 4\ \mu\text{F}$
4. C
5.  $2.5\ \mu\text{C}$
6.  $V_A = +5V, V_C = -5V$
7.  $V_{AB} = 25V, V_{BC} = 75V$
8.  $V = \frac{49}{11}V$
9. a
10. b
11. d