



Lakshya Batch 2020-21

Ch-03

Current Electricity
Formula Sheet

Sheet Credit: Anup Mohapatra

FORMULA SHEET CLASS-12 "CURRENT ELECTRICITY"

► **CHARGE :-** (SCALAR) \rightarrow constant velocity \rightarrow Current Electricity (Scalar) \rightarrow variable velocity \rightarrow Electromagnetism (UNIT = AMPERE)

► **CURRENT :-** Rate of Flow of charge = $I = \frac{Q}{t} = \frac{\text{charge}}{\text{Time}}$ (SI = Cs^{-1}) (Coulomb s^{-1})

$I_{av} = \frac{\Delta Q}{\Delta t}$ (Average) $I_{inst.} = \frac{dQ}{dt}$ (Instantaneous)

CIRCULAR PATH $\Rightarrow I = vq = \frac{ev}{2\pi r}$ (v = frequency) radius

► **DRIFT VELOCITY :-** $V_d = \frac{-eE}{m} \tau_{avg}$ $V_d = \frac{eV}{m l} \tau_{avg}$ τ_{avg} = Relaxation Time l = length.

\rightarrow Thermal velocity = $V_r = \sqrt{\frac{3k_B T}{m}}$ when V is applied in a conductor e^- move in $(-\vec{E})$ direction. τ_{mp} (k_B = Boltzmann constant)

$\rightarrow I = V_d n A$ ATT!! (n = no. of free e^- / V)

$\rightarrow \vec{j}$ = current density = $\frac{I}{A} = enV_d$


$\vec{I} = J A \cos \theta$ $I = J \cdot A$ Area vector


Assmp \rightarrow If no. of free e^- not given assume 1 atom give one free electron


► **RESISTANCE :-** $R = V/I$ (Unit = $VA^{-1} = \Omega$) (ohm) $R = \frac{m l}{ne^2 \tau A}$ $R_{net} = \frac{\rho l}{A}$

Resistivity :- $\rho = \frac{m}{ne^2 \tau}$ = depend on Temp and material not l and A (Resistivity)

► **RESISTANCES OF DIFFERENT STRUCTURE :-**

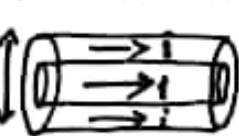$R_1 \uparrow$  $R = \frac{\rho l}{\pi(R_2^2 - R_1^2)}$

 $R = \frac{\rho l}{2\pi l} \log \frac{R_2}{R_1}$


 $R = \frac{\rho l}{\pi a b}$ $R_{net} \propto l(\text{root})$


► **OHMS LAW :-** $V_{12} = IR$ (at const temp)

$\Rightarrow V = \left(\frac{m l}{ne^2 \tau A} \right) i$ (In terms of drift velocity)


$\Rightarrow \vec{j} = \sigma \vec{E}$ ($\sigma = 1/\rho$ = conductivity)


NON OHMIC CONDUCTOR

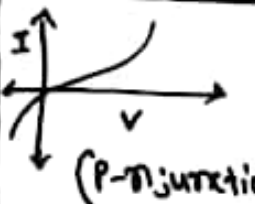
 (P-n junction)

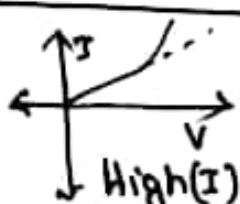 High(I)

► **CURRENT DENSITY :-** I per Area. (j)

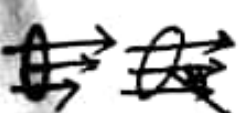 $I = \int_s \vec{j} \cdot d\vec{s}$ $I = j A \cos \theta$

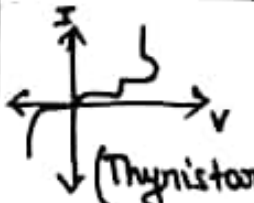 (Thyristor)

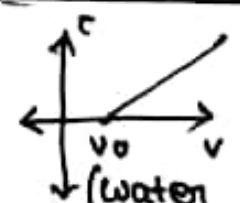 V_0 (water volt meter)

- ➔ EFFECT OF TEMPERATURE $n \uparrow$ (no. of free electron) $\tau \downarrow$ on $T \uparrow$
- Conductors $\rightarrow n \uparrow \times, \tau \uparrow, R \uparrow \uparrow$ Temp $\uparrow \uparrow$
 - Semi-conductors $\rightarrow n \uparrow R \downarrow \rho \downarrow$ as Temp $\uparrow \uparrow$
 - Alloys (Nicolme, Manganin, constantin)
- $$\int_{R_0}^{R_F} dR = \int_{T_i}^{T_F} \alpha R_0 dT$$

$\rightarrow n \uparrow \text{ and } \tau \downarrow \text{ (no change in } R)$

$$R_F = R_0 (1 - \alpha(T_F - T_i))$$
- GRAPH

$\rightarrow \alpha$ has nothing to do with coefficient of Thermal expansion

- $\alpha = \text{Temp. Coefficient of Resistance or } \rho$
- $$\alpha = \frac{R_F - R_0}{R_0 \Delta T}$$

$\alpha_{\text{copper}} \rightarrow +4 \times 10^{-3} \text{ } ^\circ\text{C}^{-1}$
 $\alpha_{\text{silicon}} \rightarrow -7 \times 10^{-2} \text{ } ^\circ\text{C}^{-1}$
 $\alpha_{\text{manganin}} \rightarrow 2 \times 10^{-6} \text{ } ^\circ\text{C}^{-1}$
- $$R_{\text{comb}} = \text{not change Temp } \uparrow \uparrow = \alpha_1 R_1 + \alpha_2 R_2 = 0$$

- SERIES COMBINATION

$$R_e = R_1 + R_2 + R_3$$

current is constant

➤ PARALLEL COMBINATION

$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

voltage Const.

- ELECTROMOTIVE FORCE (EMP)
- $$\mathcal{E} = \frac{W}{q}$$

$$V = \mathcal{E} - IR$$
 ($V = \text{Terminal voltage}$)
- Imp relation.

- KIRCHHOFF'S LAW:-
- CURRENT LAW:- Sum of current entering the junction = current leaving the junction.

$$I_1 + I_2 = I_3 + I_4$$
 (Based on Principle of conservation of charge.)
 - LOOP LAW / VOLTAGE LAW:- Algebraic sum of Potential around a closed loop is "zero". (conservation of energy)

$$\sum \Delta V = 0$$

- Direction

➤ COLOUR CODING RESISTORS

Gold	5%
Silver	10%
No	20%

➤ MOBILITY:-
Unit = $\text{m}^2\text{s}^{-1}\text{V}^{-1}$

$$\mu = \frac{V_d}{E}$$

$$\mu = \frac{q\tau}{m}$$
- BBROY of Great Britain Very Good Li Fe

MIRROR SYMMETRY

If mirror then simply remove R_e across the lines of mirror. (short circuit R_e) network

FOLDING SYMMETRY

If folding symmetry across A and B then simply fold it across A and B.

SERIES GROUPING OF CELLS :-

$$E_{eq} = E_1 + E_2 + E_3$$

$$I_{eq} = \frac{E_{eq}}{R_{eq}} = \frac{E_1 + E_2 + E_3}{R_1 + R_2 + R_3}$$

$$E_{eq} - I_{eq}R_{eq} = E_1 + E_2 + E_3 - I_{eq}(R_1 + R_2 + R_3)$$

If an external resistance is added -

$$I = \frac{V}{R_e} = \frac{nE}{nR + R_e} \quad (n \text{ in series})$$

$n \rightarrow E$ and n are connected and polarity of n are reversed then,

$$E_{eq} = (n - 2m)E \quad I_{eq} = \frac{nE}{nR + R_e}$$

PARALLEL GROUPING OF CELLS :-

$$E_{eq} = \frac{E_1 + E_2}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

For n cells in parallel \rightarrow

$$E_{eq} = E \quad R_{eq} = \frac{R}{n}$$

$$I = \frac{nE}{nR + R_e} \quad (\text{If external resistance or } R \text{ is connected.})$$

MIXED GROUPING :- (n cells in row m cell column)

$$E_{eq} = nE$$

$$R_{eq} = R + \frac{mR}{n}$$

$$I = \frac{nmE}{mR + nR}$$

$$I_{max} = \frac{nE}{2R}$$

R - external resistance

POWER :-

Energy absorbed $\rightarrow dE = Vdq$

$$1) P = I^2 R$$

$$2) P = V^2 / R$$

$$3) P = VI$$

Power absorbed (P)

$$P = \frac{dE}{dt} = \frac{Vdq}{dt}$$

$$P = VI$$

ENERGY DISSIPATED RESISTOR (HEAT)

$$E = \int P dt$$

For Pure only Resistance formula.


$$1) E = I^2 R t$$

$$2) E = V^2 / R t$$

$$3) E = V I t$$

Brightness \propto Power consumed

METRE BRIDGE (Jo by Jo)

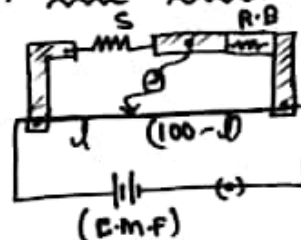


$$\frac{S}{R} = \frac{l}{(100 - l)}$$

$$\rho = \frac{SA}{l} = \frac{STW^2}{l}$$

$$\frac{\Delta R}{R} = \frac{\Delta l}{l} + \frac{100 - 4\Delta l}{(100 - l)}$$


WHEATSTONE BRIDGE :-

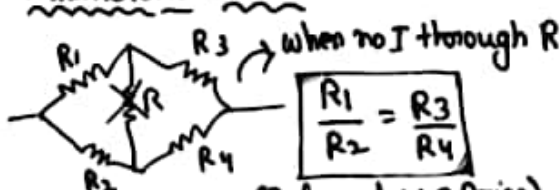

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Balanced W.S. Bridge

CONVERSION ∇ TO ∇

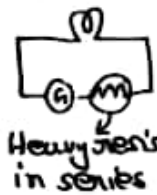

$$V = I_g (G + R)$$

V_{amm} d

Heavy resistance in series

R_{volt} ideal is always ∞

\rightarrow Measured V is small than original

CONVERSION GALVANOMETER TO AMMETER

$$I_g G = (I - I_g) S$$

$\rightarrow S$ - Shunt (small resistance)

$$R_{amm} = \frac{GS}{G + S}$$

R_{amm} ideal is always equal to ZERO

\rightarrow Measured current is always small than original

POTENTIOMETER :-

$$V_{ac} = \frac{V}{l} x$$

x = length of which V
 l = original length

Comparison of EMF :-

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$


$$K = \frac{V}{l} \quad \text{Potential gradient}$$

Internal resistance :-

$$r = R \left(\frac{E}{V} - 1 \right)$$

Battery EMF

Cell's EMF

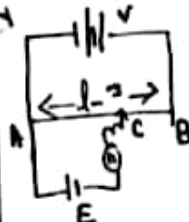

Efficiency Source EMF

$$\eta = \frac{R}{R + r} = \frac{P_{out}}{P_{in}}$$

$$\eta_{max} = 50\%$$

$$\max P = \frac{E^2}{4R}$$

FUSE :- Heat produced / Per unit t = Heat radiated per unit t

$$I^2 = K \theta^3$$

\rightarrow Some constant.