



## Ch—07 Alternating Current

### Daily Practice Problem 06

**Q1.** Determine the impedance of a series LCR-circuit if the reactance of  $C$  and  $L$  are  $250 \Omega$  and  $220 \Omega$  respectively and  $R$  is  $40 \Omega$ .


**Q2.** A resistor of  $12 \text{ ohm}$ , a capacitor of reactance  $14 \text{ ohm}$  and a pure inductor of inductance  $0.1 \text{ henry}$  are joined in series and placed across a  $200 \text{ volt}$ ,  $50 \text{ Hz}$  a.c. supply. Calculate

- the current in the circuit and
- the phase angle between the current and the voltage. Take  $\pi = 3$  for purpose of calculations.

**Q3.** A  $50 \mu\text{F}$  capacitor,  $0.05 \text{ H}$  inductor and a  $48 \Omega$  resistor are connected in series with an a.c. source of emf,  $\epsilon = 310 \sin 314 t$ . Calculate the reactance of the circuit and tell its nature. What is the phase angle between the current and the applied emf?

**Q4.** A  $12 \Omega$  resistance and an inductance of  $0.05 / \pi \text{ H}$  with negligible resistance are connected in series. Across the ends of this is connected a  $130 \text{ V}$  alternating voltage of frequency  $50 \text{ Hz}$ . Calculate the alternating current in the circuit and the potential difference across the resistance and across the inductance.

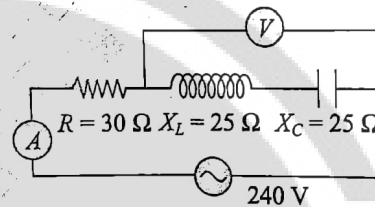**Q5.** In the circuit shown in the figure neglecting source resistance the voltmeter and ammeter reading will respectively, will be



- $0 \text{ V}$ ,  $3 \text{ A}$
- $150 \text{ V}$ ,  $3 \text{ A}$
- $150 \text{ V}$ ,  $6 \text{ A}$
- $0 \text{ V}$ ,  $8 \text{ A}$

**Q6.** An LCR-series circuit with  $L = 100 \text{ mH}$ ,  $C = 100 \mu\text{F}$ ,  $R = 120 \Omega$ . is connected to an a.c. source of emf  $\epsilon = 30 \sin 100 t \text{ volt}$ . Find the impedance, peak current and resonant frequency of the circuit.

**Q7.** A circuit connected to an AC source of emf  $e = e_0 \sin(100t)$  with  $t$  in seconds, gives a phase difference of  $\frac{\pi}{4}$  between the emf  $e$  and current  $i$ . Which of the following circuits will exhibit this?

- RC circuit with  $R = 1 \text{ k}\Omega$  and  $C = 1 \mu\text{F}$

b.  $RL$  circuit with  $R = 1\text{ k}\Omega$  and  $L = 1\text{ mH}$

d.  $RL$  circuit with  $R = 1\text{ k}\Omega$  and  $L = 10\text{ mH}$

c.  $RC$  circuit with  $R = 1\text{ k}\Omega$  and  $C = 10\text{ }\mu\text{F}$

---

## ANSWERS

1.  $50\text{ }\Omega$

4.  $10\text{ A}$ ,  $120\text{ V}$ ,  $50\text{ V}$

7. c

2.  $10\text{ A}$ ,  $53.1^\circ$

5. d

3.  
 $48\text{ }\Omega$ ,  $45^\circ$  (current leads voltage)

6.  $150\text{ }\Omega$ ,  $0.2\text{ A}$ ,  $50\text{ Hz}$