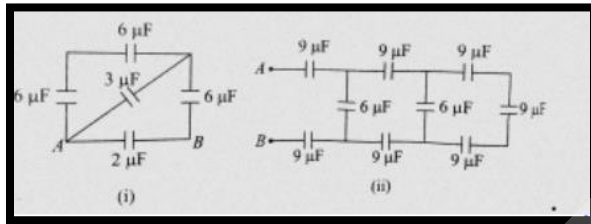



## Ch—02 Electrostatic Potential and Capacitance

### Daily Practice Problem 07

**Q1.** In figure, different capacitors are arranged. Find the equivalent capacity across the points A and B.



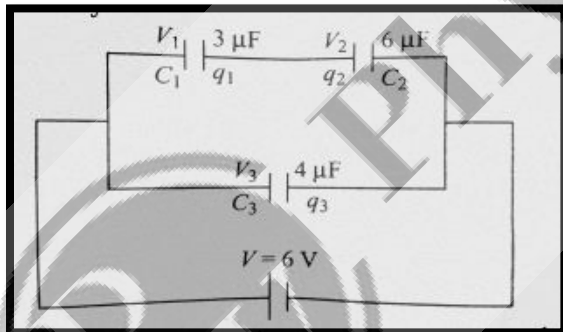**Q2.** Three capacitors of capacitances  $3 \mu\text{F}$ ,  $6 \mu\text{F}$ , and  $4 \mu\text{F}$  are connected as shown across a battery of emf  $6 \text{ V}$ .




- (i) Find the equivalent capacitance.
- (ii) Find the potential difference and charge on each capacitor.
- (iii) Find the energy stored in each capacitor and the total energy stored in the system of capacitors.

**Q3.** Three capacitors of equal capacitance, when connected in series have net capacitance  $C_1$ , and when connected in parallel have net capacitance  $C_2$ . What is the value of  $C_1/C_2$ ?


**Q4.** Two capacitors of capacitance of  $6 \mu\text{F}$  and  $12 \mu\text{F}$  are connected in series with a battery. The voltage across the  $6 \mu\text{F}$  capacitor is  $2 \text{ V}$ . Compute the total battery voltage.

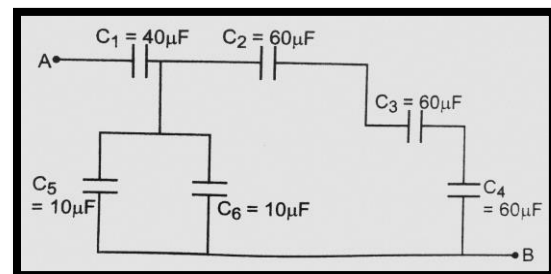**Q5.** Find the equivalent capacitance of the combination of capacitors between the points A and B as shown in Fig.. Also calculate the total charge that flows in the circuit when a  $100 \text{ V}$  battery is connected between the points A and B.




**Q6.** Seven capacitors, each of capacitance  $2 \mu\text{F}$  are to be connected in a configuration to obtain an effective capacitance of  $10/11 \mu\text{F}$ . Suggest a suitable combination to achieve the desired result.

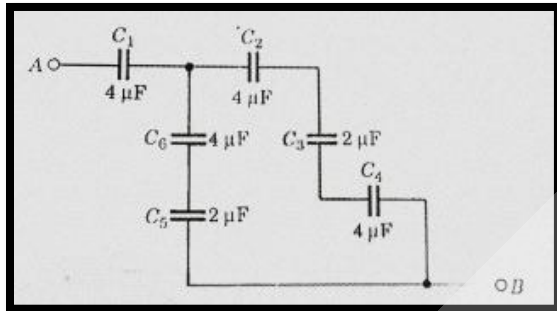**Q7.** Calculate the equivalent capacitance points A and B of the circuit given below




**Q8.** If  $C_1 = 20 \mu\text{F}$ ,  $C_2 = 30 \mu\text{F}$  and  $C_3 = 15 \mu\text{F}$  and the insulated plate of  $C_1$  be at a potential of  $90 \text{ V}$ , one plate of  $C_3$  being earthed. What is the potential difference between the plates of  $C_2$ , three capacitors being connected in series?

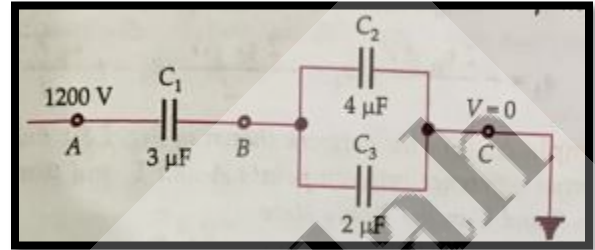
**Q9.** In the circuit shown if the point C is earthed and point A is given a potential of  $+1200 \text{ V}$ , find the charge on each capacitor and potential at B.



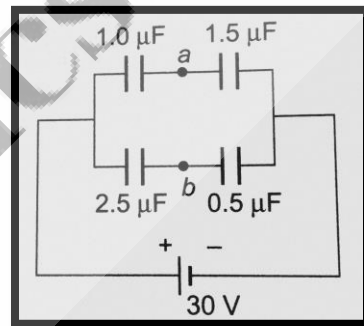
**Q10.** Four capacitors are connected as shown in figure to a  $30 \text{ V}$  battery. Find the potential difference between points a and b.



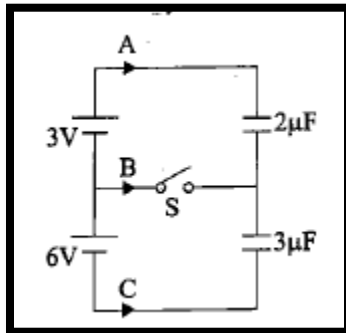
**Q11.** What charges will flow through section B of the circuit in the direction shown when switch S is closed.



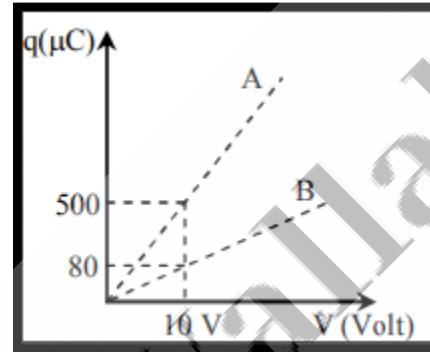**Q13.** Figure shows charge ( $q$ ) versus voltage ( $V$ ) graph for series and parallel combination of two given capacitors. The capacitances are



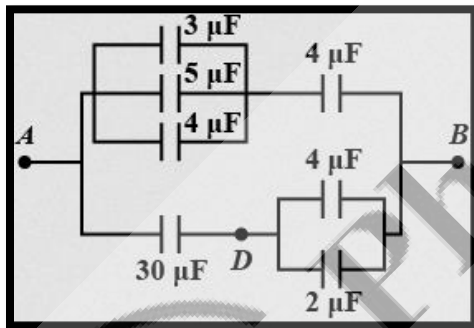**Q12.** Figure shows a network of seven capacitors. If charge on  $5\ \mu\text{F}$  capacitor is  $10\ \mu\text{C}$ , find the potential difference between points A and C



- $60\ \mu\text{F}$  and  $40\ \mu\text{F}$
- $50\ \mu\text{F}$  and  $30\ \mu\text{F}$
- $20\ \mu\text{F}$  and  $30\ \mu\text{F}$
- $40\ \mu\text{F}$  and  $10\ \mu\text{F}$

**ANSWERS**

1. (i)  $5\mu\text{F}$ , (ii)  $3\mu\text{F}$

2. (i)  $6\mu\text{F}$  (ii)  $V_1 = 4\text{V}, V_2 = 2\text{V}$ ,

$$q_1 = 12\mu\text{C}, q_2 = 12\mu\text{C}, q_3 = 24\mu\text{C}$$

(iii)  $U_1 = 24\mu\text{J}, U_2 = 12\mu\text{J}, U_3 = 72\mu\text{J}$

$$U = 108\mu\text{J}$$

3.  $\frac{C_1}{C_2} = \frac{1}{9}$

4.  $3\text{V}$

5.  $C = 20\mu\text{F}, q = 2\text{mC}$

6. Parallel combination of 5 capacitors in series with the other 2 capacitors

7.  $\frac{28}{19}\mu\text{F}$

8.  $20\text{V}$

9.  $q_1 = 2.4 \times 10^{-3}\text{C}, q_2 = 1.6 \times 10^{-3}\text{C},$

$$q_3 = 0.8 \times 10^{-3}\text{C}, V_B = 400\text{V}$$

10.  $13\text{V}$

11.  $120\mu\text{C}$

12.  $5.33\text{V}$

13. d