



## Ch—07 Alternating Current

### Daily Practice Problem 08

**Q1.** A  $1.0 \mu F$  capacitor is charged by a  $40.0 V$  power supply. The fully charged capacitor is then discharged through a  $10.0 mH$  inductor. Find the maximum current in the resulting oscillations.

**Q2.** A  $10 \mu F$  capacitor is charged to a potential of  $25 V$ . The battery is then disconnected and pure  $100 mH$  coil is connected across the capacitor so that LC-oscillations are set up. Calculate the maximum current in the coil.

**Q3.** A  $1.5 mH$  inductor in an LC-circuit stores a maximum energy of  $30 \mu J$ . What is the maximum current in the circuit?

**Q4.** In an oscillatory circuit, the self-inductance of the coil used is  $10 mH$ . If the oscillatory frequency of the circuit is  $1.0 MHz$ , find the capacitance of the capacitor connected in the circuit.

**Q5.** A wave of wavelength  $300 m$  can be radiated through a transmitter. A capacitor of capacitance  $2.4 \mu F$  is available. What is the inductance of the coil required for the oscillatory circuit?

---

**ANSWERS**

1.  $40.0\text{ mA}$

2.  $0.25\text{ A}$

3.  $0.2\text{ A}$

4.  $2.53\text{ }\mu\text{F}$

5.  $1.056 \times 10^{-8}\text{ H}$

