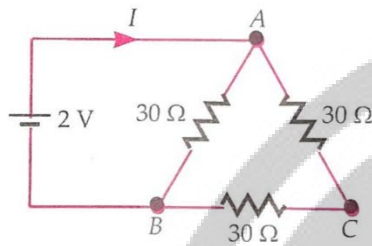



Ch—03 Current Electricity

Daily Practice Problem 04


Q1. Find the value of current I in the circuit shown in Fig.



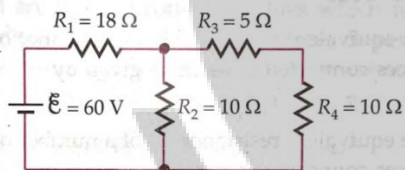
Q2. Determine the voltage drop across the resistor R_1 in the circuit given below with $E = 60\text{ V}$, $R_1 = 18\ \Omega$, $R_2 = 10\ \Omega$.



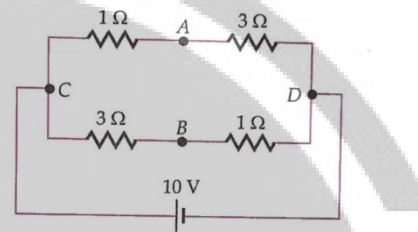
Q4. A battery of emf 10 V is connected to resistances as shown in Fig. Find the potential difference between the points A and B.



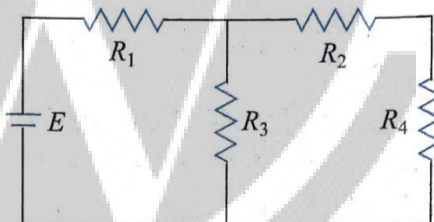
Q5. Determine the voltage drop across the resistor R_1 in the circuit given below with $E = 65\text{ V}$, $R_1 = 50\ \Omega$, $R_2 = 100\ \Omega$, $R_3 = 100\ \Omega$, and $R_4 = 300\ \Omega$.



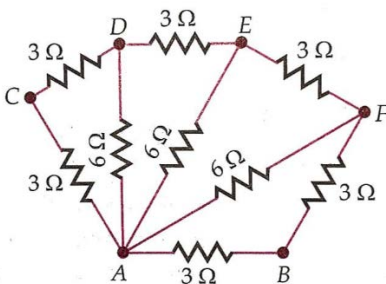
Q3. Find the effective resistance between points A and B for the network shown in Fig



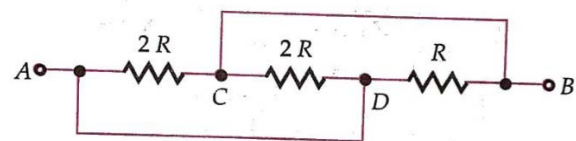
Q6. What is the equivalent resistance between points A and B of the circuit shown in Fig.?



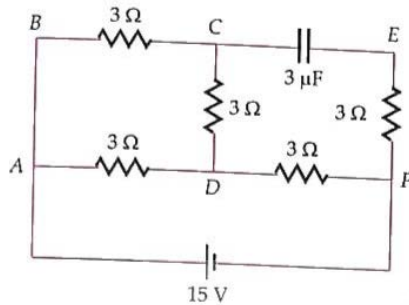
Q7. In the circuit shown in Fig., find the potential difference across the capacitor.



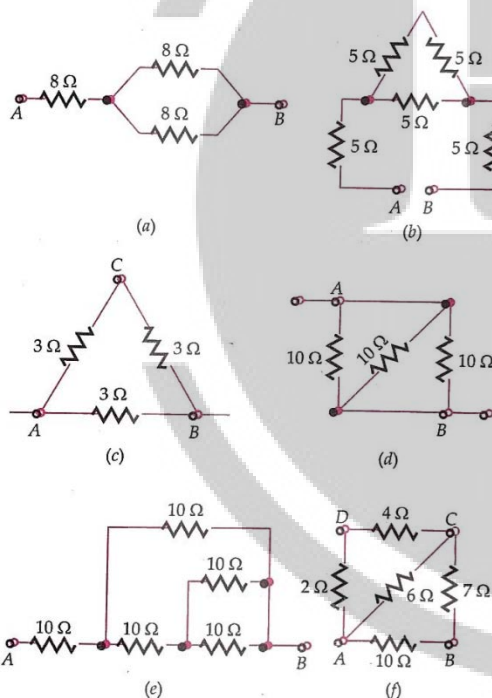
Q8. Calculate the equivalent resistance between points A and B in each of the following networks of resistors:



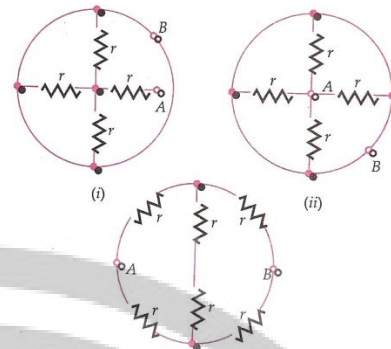
Q9. Find the equivalent resistance of the networks shown in Fig. between the points A and B.



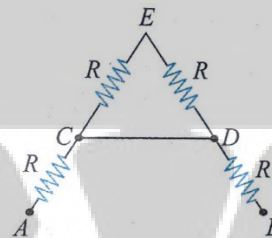Q10. Four identical resistance each having value R are arranged as shown in figure. Find the equivalent resistance between A and B



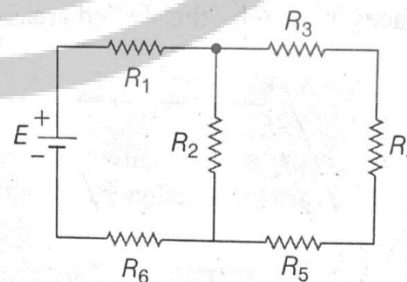Q11. In the figure shown, what is the current (in ampere) drawn from the battery? You are given: $R_1 = 15\ \Omega$, $R_2 = 10\ \Omega$, $R_3 = 20\ \Omega$, $R_4 = 5\ \Omega$, $R_5 = 25\ \Omega$, $R_6 = 30\ \Omega$, $E = 15V$



- (a) $13/24$
- (b) $7/18$
- (c) $20/3$
- (d) $9/32$

ANSWERS

1. 0.1 A

2. 45 V

3. $2\ \Omega$

4. 5.0 V

5. 25 V

6. $R/2$

7. 12 V

8. a. $12\ \Omega$ b. $40/3\ \Omega$ c. $2\ \Omega$ d. $10/3\ \Omega$ e. $16\ \Omega$
f. $5\ \Omega$

9. a. $4/3\ r$ b. $r/4$ c. r

10. $2R$

11. d