

Ch—03 Current Electricity

Daily Practice Problem 09

Q1. What is the value of the shunt that passes 10% of the main current through a galvanometer of $99\ \Omega$?

Q2. The deflection in a moving coil galvanometer falls from 50 divisions to 10 divisions when a shunt of $12\ \Omega$ is applied. What is the resistance of the galvanometer? Assume the main current to remain same.

Q3. The scale of a galvanometer is divided into 150 equal divisions. The galvanometer has a current sensitivity of 10 divisions per mA and a voltage sensitivity of 2 divisions per mV. How can the galvanometer be designed to read

- (i) 6 A per division and
- (ii) 1 V per division?

Q4. A galvanometer has a resistance of $50\ \Omega$ and its full-scale deflection current is $50\ \mu\text{A}$. What resistance should be added to it so that it can have a range of 0-5 V?

Q5. A voltmeter reads 5.0 V at full-scale deflection and is graded according to its resistance per volt at full-scale deflection as $5000\ \Omega\text{V}^{-1}$. How will you convert it into a voltmeter that reads 20 V at full-scale deflection? Will it still be graded as $5000\ \Omega\text{V}^{-1}$? Will you prefer this voltmeter to one that is graded $2000\ \Omega\text{V}^{-1}$?


Q6. A moving coil galvanometer when shunted with a resistance of $5\ \Omega$ gives a full scale deflection for 250 mA and when a resistance of $1050\ \Omega$ is connected in series, it gives a full scale deflection for 25 volt. Find the resistance of the galvanometer

Q7. A galvanometer can be converted into a voltmeter of certain range by connecting a resistance of $980\ \Omega$ in series with it. When the resistance is $470\ \Omega$ connected in series, the range is halved. Find the resistance of the galvanometer.


Q8. The deflection produced in a galvanometer is reduced to 45 divisions from 55 when a shunt of $8\ \Omega$ is used. Calculate the resistance of the galvanometer.

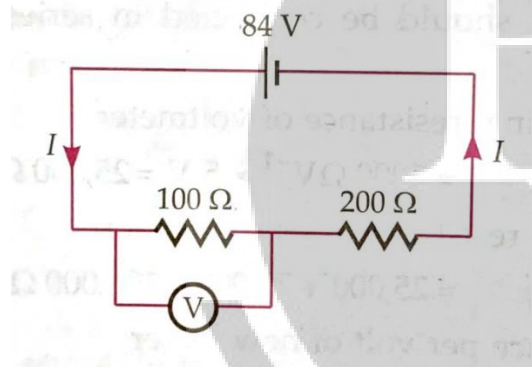Q9. A voltmeter V of resistance $400\ \Omega$ is used to measure the potential difference across a $100\ \Omega$ resistor in the circuit shown in Fig.

- What will be the reading on the voltmeter?
- Calculate the potential difference across $100\ \Omega$ resistor before the voltmeter is connected.



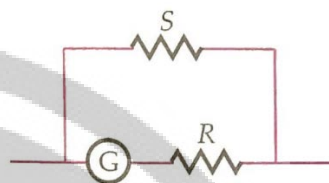Q10. A galvanometer has a resistance of $8\ \Omega$. It gives a full-scale deflection for a current of $10\ \text{mA}$. It is to be converted into an ammeter of range $5\ \text{A}$. The only shunt resistance available is of $0.02\ \Omega$, which is not suitable for this conversion. Find the value of resistance R that must be connected in series with the galvanometer (Fig.) to get ammeter of desired range.



Q11. A galvanometer having a resistance of $20\ \Omega$ and 30 divisions on both sides has figure of merit $0.005\ \text{ampere/division}$. The resistance that should be connected in series such that it can be used as a voltmeter upto $15\ \text{volt}$ is

- $100\ \Omega$
- $125\ \Omega$
- $120\ \Omega$
- $80\ \Omega$

ANSWERS

1. 11Ω

7. 40Ω

2. 48Ω

8. 36Ω

3. (i) $8.3 \times 10^{-5}\Omega$

(ii) 9995Ω

9. (i) 24V

(ii) 28V

4. 100 k Ω

10. 1.98Ω

5. 75,000 Ω ; YES; NO

11. d

6. 50Ω